# Project 4: Vending Machine


Haley Kim 405111152

## **Introduction and Requirement**

The vending machine for this project is a Moore machine whose output only relies on the current state of the machine, regardless of the input fed in. The inputs help determine the current state, and the current state determines the output. The vending machine needs to be able to handle each input and adjust its four outputs accordingly in order to represent the state that the machine is in.

This project has eight inputs it must recognize and handle:

 - 1. CARD IN: remains high as long as card is inserted
- 2. VALID TRAN: signal displaying validity of card
- 3. ITEM CODE: 4 bit signal for one digit of the item code
- 4. KEY PRESS: ITEM CODE valid for reading when signal is high
- 5. DOOR OPEN: high to indicate an open door
- 6. RELOAD: to reload machine when high
- 7. CLK: 100 MHz clock with 10ns period
- 8. RESET: to reset machine when high



High-Level Explanation of FSM Diagram:

The vending machine must be able to recognize that a card was inserted, then wait for the user's input for the two digits of the item code. If the item code is not received, the machine stops the transaction and returns to its idle state. If the received item code is valid and that item is in stock, the machine must wait for the VALID\_TRAN signal to come from the bank. If the signal is not received, the machine must indicate that the transaction failed. If the signal is received, the machine must vend and decrement the item counter. If the door does not open, the machine returns to the idle state. If the door opens, the machine must wait for the door to close again before returning to the idle state.

## **Design Description**

```
The main overarching module is vending machine, with inputs:
```

```
CARD_IN,
VALID_TRAN,
[3:0] ITEM_CODE,
KEY_PRESS,
DOOR_OPEN,
RELOAD,
CLK,
RESET,
```

## and outputs:

```
VEND,
INVALID_SEL,
FAILED_TRAN,
[2:0] COST
```

Main module vending machine does not call any submodules.

```
vending_machine's logic:
```

```
always block #1:

if RESET is high, sets current_state to RESET_STATE
otherwise, sets current_state as next_state
always block #2:

for the 4 states that could timeout, increment counter


(TRANSACT_STATE_1, TRANSACT_STATE_2,
WAIT_VALID_SIGNAL_STATE, VEND_STATE)
for other states, set counter to 0
```


```
if current state is not next state, set counter to 0 (for a fresh counter start on state
      changes)
always block #3:
      **implementing the fsm diagram state transitions in verilog code**
      **for the 4 states with possible timeouts, next state determined by both counter
             AND inputs**
      **for the other states, next state determined by inputs**
      if current state is IDLE STATE:
             if CARD IN is high, go to TRANSACT STATE 1
             if RELOAD is high, go to RELOAD STATE
             otherwise, remain in IDLE STATE
      if current state is RESET STATE:
             if RESET is low, go to IDLE STATE
             otherwise, remain in RESET STATE
      if current state is RELOAD STATE:
             if RELOAD is low, go to IDLE STATE
             otherwise, remain in RELOAD STATE
      if current state is TRANSACT STATE 1:
             if counter is at 5, timeout, and go to IDLE STATE
             if counter is less than 5,
                    if KEY PRESS is high,
                           store ITEM CODE in MSD for later
                           go to TRANSACT STATE 2
                    otherwise, remain in TRANSACT STATE 1
      if current state is TRANSACT STATE 2:
             if counter is at 5, timeout, and go to IDLE STATE
             if counter is less than 5,
                    if KEY_PRESS is high,
                           store ITEM CODE in LSD
                           if the item code represented by MSD and LSD are invalid,
                                 go to INVALID SEL STATE
                           if the item code represented by MSD and LSD are valid but
                           the item counter for that item is 0,
                                 go to INVALID SEL STATE
                           otherwise, go to WAIT VALID SIGNAL STATE
                    otherwise, remain in TRANSACT STATE 2
      if current state is INVALID SEL STATE:
             go to IDLE STATE
      if current state is WAIT VALID SIGNAL STATE:
             if counter is at 5, timeout, and go to INVALID TRAN STATE
```

```
if VALID TRAN is high,
                          go to VEND STATE
                    otherwise, remain in WAIT_VALID_SIGNAL_STATE
      if current state is VEND STATE:
             if counter is at 5, timeout, and go to IDLE STATE
             if counter is less than 5,
                    if DOOR OPEN is high,
                          go to DOOR HIGH STATE
                    otherwise, remain in VEND STATE
      if current state is INVALID TRAN STATE:
             go to IDLE STATE
      if current state is DOOR HIGH STATE:
             if DOOR OPEN is low, go to IDLE STATE
             otherwise, remain in DOOR_HIGH_STATE
always block #4:
      **set outputs based on current_state**
      if current state is IDLE STATE:
             set all 4 outputs to 0
      if current state is RESET STATE:
             set all 4 outputs to 0
             set all 20 item counters to 0
      if current state is RELOAD STATE:
             set all 20 item counters to 10
      if current state is TRANSACT STATE 1:
             do nothing
      if current state is TRANSACT STATE 2:
             do nothing
      if current state is INVALID SEL STATE:
             set INVALID SEL to high
      if current state is WAIT VALID SIGNAL STATE:
             based on item code, set appropriate COST
      if current state is VEND STATE:
             set VEND to high
             decrement appropriate item counter based on item code
      if current state is INVALID TRAN_STATE:
             set FAILED TRAN to high
      if current state is DOOR HIGH STATE:
             do nothing
```

if counter is less than 5,

## **Simulation Documentation**

 

 

## RTL Schematic:

From the RTL Schematic, it is obvious that the design is much more complex than either lab 1 or lab 2. It is also evident that my design is not very modular, since the schematic is huge each element is an individual mux or gate. It is quite impossible to take in much information from the full schematic because everything is so broken down.

vending_machine Project Status					
Project File:	Proj4.xise	Parser Errors:	No Errors		
Module Name:	vending_machine	Implementation State:	Placed and Routed		
Target Device:	xc6slx4-3tqg144	• Errors:	No Errors		
Product Version:	ISE 14.7	Warnings:	139 Warnings (115 new)		
Design Goal:	Balanced	Routing Results:	All Signals Completely Routed		
Design Strategy:	Xilinx Default (unlocked)	Timing Constraints:	All Constraints Met		
Environment:	System Settings	• Final Timing Score:	0 (Timing Report)		

Device Utilization Summary					
Slice Logic Utilization	Used	Available	Utilization	Note(s)	
Number of Slice Registers	94	4,800	1%		
Number used as Flip Flops	10				
Number used as Latches	84				
Number used as Latch-thrus	0				
Number used as AND/OR logics	0				
Number of Slice LUTs	116	2,400	4%		
Number used as logic	115	2,400	4%		
Number using O6 output only	71				
Number using O5 output only	0				
Number using O5 and O6	44				
Number used as ROM	0				
Number used as Memory	0	1,200	0%		
Number used exclusively as route-thrus	1				
Number with same-slice register load	1				
Number with same-slice carry load	0				
Number with other load	0				
Number of occupied Slices	40	600	6%		
Number of MUXCYs used	0	1,200	0%		
Number of LUT Flip Flop pairs used	135				
Number with an unused Flip Flop	42	135	31%		
Number with an unused LUT	19	135	14%		
Number of fully used LUT-FF pairs	74	135	54%		
Number of unique control sets	23				
Number of slice register sites lost to control set restrictions	90	4,800	1%		
Number of bonded <u>IOBs</u>	40	102	39%		
IOB Flip Flops	4				

IOB Latches	18			
Number of RAMB16BWERs	0	12	0%	
Number of RAMB8BWERs	0	24	0%	
Number of BUFIO2/BUFIO2_2CLKs	0	32	0%	
Number of BUFIO2FB/BUFIO2FB_2CLKs	0	32	0%	
Number of BUFG/BUFGMUXs	1	16	6%	
Number used as BUFGs	1			
Number used as BUFGMUX	0			
Number of DCM/DCM_CLKGENs	0	4	0%	
Number of ILOGIC2/ISERDES2s	4	200	2%	
Number used as ILOGIC2s	4			
Number used as ISERDES2s	0			
Number of IODELAY2/IODRP2/IODRP2_MCBs	0	200	0%	
Number of OLOGIC2/OSERDES2s	18	200	9%	
Number used as OLOGIC2s	18			
Number used as OSERDES2s	0			
Number of BSCANs	0	4	0%	
Number of BUFHs	0	128	0%	
Number of BUFPLLs	0	8	0%	
Number of BUFPLL_MCBs	0	4	0%	
Number of DSP48A1s	0	8	0%	
Number of ICAPs	0	1	0%	
Number of PCILOGICSEs	0	2	0%	
Number of PLL_ADVs	0	2	0%	
Number of PMVs	0	1	0%	
Number of STARTUPs	0	1	0%	
Number of SUSPEND_SYNCs	0	1	0%	
Number of SOSPEND_STRCS	"	-	0,0	

Performance Summary				ы
Final Timing Score:	0 (Setup: 0, Hold: 0)	Pinout Data:	Pinout Report	
Routing Results:	All Signals Completely Routed	Clock Data:	Clock Report	
Timing Constraints:	All Constraints Met			

Detailed Reports					Ŀ
Report Name	Status	Generated	Errors	Warnings	Infos
Synthesis Report	Current	Fri Dec 11 23:20:12 2020	0	114 Warnings (90 new)	2 Infos (2 new)
Translation Report	Current	Fri Dec 11 23:20:21 2020	0	0	0
Map Report	Current	Fri Dec 11 23:20:34 2020	0	25 Warnings (25 new)	6 Infos (6 new)
Place and Route Report	Current	Fri Dec 11 23:20:41 2020	0	0	3 Infos (3 new)
Power Report					
Post-PAR Static Timing Report	Current	Fri Dec 11 23:20:45 2020	0	0	4 Infos (4 new)
Bitgen Report					

Secondary Reports			ы
Report Name	Status	Generated	
ISIM Simulator Log	Out of Date	Fri Dec 11 23:19:55 2020	

Date Generated: 12/12/2020 - 04:53:54

## Design Summary Report:

The design was synthesized with no errors. Other than this crucial information, the design summary report gives us how many of each part was utilized for the synthesis.

```
______
HDL Synthesis Report
Macro Statistics
                                                                                                                                                                        : 1
  16x7-bit single-port Read Only RAM
                                                                                                                                                                      : 1
# Adders/Subtractors
                                                                                                                                                                        : 19
  3-bit adder
                                                                                                                                                                        : 1
  4-bit subtractor
                                                                                                                                                                      : 18
# Registers
                                                                                                                                                                        : 2
  3-bit register
                                                                                                                                                                        : 1
  4-bit register
                                                                                                                                                                        : 1
# Latches
                                                                                                                                                                        : 90
                                                                                                                                                                       : 90
  1-bit latch
# Comparators
                                                                                                                                                                        : 3
  4-bit comparator equal
                                                                                                                                                                      : 1
  4-bit comparator greater
                                                                                                                                                                      : 2
# Multiplexers
                                                                                                                                                                        : 249
  1-bit 2-to-1 multiplexer
                                                                                                                                                                        : 232
  4-bit 2-to-1 multiplexer
_____
_____
                                                                     Advanced HDL Synthesis
______
Total REAL time to Xst completion: 5.00 secs
Total CPU time to Xst completion: 4.76 secs
Total memory usage is 485720 kilobytes
Number of errors : 0 (
                                                                                            0 filtered)
Number of warnings: 114 ( 0 filtered)
Number of infos: 2 ( 0 filtered)
  ______
 Timing Report
  NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.
                    FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT
                    GENERATED AFTER PLACE-and-ROUTE.
  Clock Information:
                                                                                                                                                                                                                              | Clock buffer(FF name) | Load |
  Clock Signal
  current_state[3]_GND_6_o_Mux_143_o(Mmux_current_state[3]_GND_6_o_Mux_143_o11:0) | NONE(*)(LSD_3) | 8
  current_state[3]_GND_10_o_Mux_151_o(Mmux_current_state[3]_GND_10_o_Mux_151_o11:0)| NONE(*)(MSD_3)
                                                                                                                                                                                                                                               NONE(*)(FAILED_TRAN) | 1
NONE(*)(VEND) | 1
  Mram__n11494(Mram__n114941:0)
  Mram__n11492(Mram__n114921:0)
                                                                                                                                                                                                                                                NONE(*)(INVALID_SEL)
  Mram__n1149(Mram__n114911:0)
                                                                                                                                                                                                                                                                                                                    1 1
 | NONE(*)(ITEM_COUNT_03_2)| 4| current_state[3]_GND_28_o_Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o_0Mux_541_o
 current_state[3]_GND_80_o_Mux_645_o(Mmux_current_state[3]_GND_80_o_Mux_645_o(2:0)| NONE(*)(ITEM_COUNT_16_2)| 4
current_state[3]_GND_72_o_Mux_629_o(Mmux_current_state[3]_GND_72_o_Mux_629_o1:0)| NONE(*)(ITEM_COUNT_14_2)| 4
 current_state[3]_GND_68_o_Mux_621_o(Mmux_current_state[3]_GND_68_o_Mux_621_o11:0)| NONE(*)(ITEM_COUNT_12_2)| 4
current_state[3]_GND_64_o_Mux_631_o(Mmux_current_state[3]_GND_64_o_Mux_631_o12:0)| NONE(*)(ITEM_COUNT_12_2)| 4
current_state[3]_GND_24_o_Mux_533_o(Mmux_current_state[3]_GND_24_o_Mux_533_o11:0)| NONE(*)(ITEM_COUNT_02_2)| 4
current_state[3]_GND_92_o_Mux_669_o(Mmux_current_state[3]_GND_92_o_Mux_669_o1:0)| NONE(*)(ITEM_COUNT_19_1)| 4
current_state[3]_GND_76 o Mux 637 o(Mmux_current_state[3]_GND_76 o Mux_637 o(Mmux_curr
```

## HDL Synthesis Report:

This report tells us which parts were utilized for the synthesis of this project. A large number of multiplexers are used, a total of 249, which is significantly lower than the number of multiplexers used for project 3. Unlike project 3 which used a 4x4 read only RAM, project 4 used a 16x7 read only RAM. The fact that all logic were in always blocks with no submodules and a overall simpler structure may have actually saved up on parts. Unlike previous projects, the Synthesis Report for this project also included a very long Timing Report, which went into great detail about the CLK implemented as well as timing constraints.

#### Design Summary Number of errors: Number of warnings: 25 Slice Logic Utilization: Number of Slice Registers: 94 out of 4,800 1% Number used as Flip Flops: 10 Number used as Latches: 84 Number used as Latch-thrus: Number used as AND/OR logics: 0 0 2,400 Number of Slice LUTs: 116 out of 4% Number used as logic: 115 out of 2,400 4% Number using 06 output only: 71 Number using 05 output only: 0 Number using 05 and 06: 44 Number used as ROM: 0 Number used as Memory: 0 out of 1,200 0% Number used exclusively as route-thrus: 1 Number with same-slice register load: 1 0 Number with same-slice carry load: Number with other load: 0

Slice Logic Distribution:			
Number of occupied Slices:	40 out of	600	6%
Number of MUXCYs used:	0 out of	1,200	0%
Number of LUT Flip Flop pairs used:	135		
Number with an unused Flip Flop:	42 out of	135	31%
Number with an unused LUT:	19 out of	135	14%
Number of fully used LUT-FF pairs:	74 out of	135	54%
Number of unique control sets:	23		
Number of slice register sites lost			
to control set restrictions:	90 out of	4,800	1%

A LUT Flip Flop pair for this architecture represents one LUT paired with one Flip Flop within a slice. A control set is a unique combination of clock, reset, set, and enable signals for a registered element. The Slice Logic Distribution report is not meaningful if the design is over-mapped for a non-slice resource or if Placement fails.

Number used as BUFGs: Number used as BUFGMUX:	1		
Number of DCM/DCM CLKGENs:	0 out of	4	0%
Number of ILOGIC2/ISERDES2s:	0 out of	200	0%
Number of IODELAY2/IODRP2/IODRP2_MCBs:	0 out of	200	0%
Number of OLOGIC2/OSERDES2s:	4 out of	200	2%
Number used as OLOGIC2s:	4		
Number used as OSERDES2s:	0		
Number of BSCANs:	0 out of	4	0%
Number of BUFHs:	0 out of	128	0%
Number of BUFPLLs:	0 out of	8	0%
Number of BUFPLL_MCBs:	0 out of	4	0%
Number of DSP48A1s:	0 out of	8	0%
Number of ICAPs:	0 out of	1	0%
Number of PCILOGICSEs:	0 out of	2	0%
Number of PLL_ADVs:	0 out of	2	0%
Number of PMVs:	0 out of	1	0%
Number of STARTUPs:	0 out of	1	0%
Number of SUSPEND_SYNCs:	0 out of	1	0%

Average Fanout of Non-Clock Nets: 4.30

IO Utilization:

 Number of bonded IOBs:
 40 out of
 102 39%

 IOB Flip Flops:
 4

 IOB Latches:
 18

Average Fanout of Non-Clock Nets: 3.27

Peak Memory Usage: 762 MB

Total REAL time to MAP completion: 9 secs Total CPU time to MAP completion: 8 secs

## Map Report:

While other information is similar to that given by the HDL Synthesis Report and Design Summary Report, the Map Report uniquely identifies the peak memory usage and the total REAL time to MAP completion. The total REAL time to completion is lesser by 1 second compared to that of project 3, which is not that great of a difference. The two projects have a similar level of complexity, so this similarity makes sense. Overall, this project did not consume as many parts as I anticipated.

```
Starting initial Timing Analysis. REAL time: 2 secs
Finished initial Timing Analysis. REAL time: 2 secs
Starting Router
Phase 1 : 796 unrouted;
                              REAL time: 2 secs
Phase 2 : 722 unrouted;
                              REAL time: 3 secs
Phase 3 : 347 unrouted;
                             REAL time: 3 secs
Phase 4 : 346 unrouted; (Par is working to improve performance)
                                                                    REAL time: 3 secs
Updating file: vending_machine.ncd with current fully routed design.
Phase 5 : 0 unrouted; (Par is working to improve performance)
                                                                  REAL time: 3 secs
Phase 6 : 0 unrouted; (Par is working to improve performance)
                                                                  REAL time: 3 secs
Phase 7 : 0 unrouted; (Par is working to improve performance)
                                                                  REAL time: 3 secs
Phase 8 : 0 unrouted; (Par is working to improve performance)
                                                                  REAL time: 3 secs
Phase 9 : 0 unrouted; (Par is working to improve performance)
                                                                  REAL time: 3 secs
Phase 10 : 0 unrouted; (Par is working to improve performance)
                                                                  REAL time: 3 secs
Total REAL time to Router completion: 3 secs
Total CPU time to Router completion: 3 secs
```


### Place and Route Report:

While the other information given by the Place and Route Report overlaps with the HDL Synthesis Report, the Design Summary Report, and the Map Report, the Place and Routee Report alone gives us information about the phases taken to route, and the REAL time it took. For this specific design, routing was completed in 4 phases, and 11 seconds REAL time.



// zoomed out, entire view


Test Case 1: RESET

 

- when RESET is high, the fsm appropriately enters the RESET STATE (0001)
- returns back to IDLE STATE(0000) when RESET is low
- all outputs are set to 0
- ITEM\_COUNT\_14 is set to 0 (thus, all item counters must be set to zero 14 was the only one I displayed for debugging purposes)


- the second time RESET goes high, it remains in the RESET\_STATE for as long as RESET is high

Test Case 2: RELOAD

 


- when RELOAD is high, the fsm appropriate enters the RELOAD STATE(0010)
- returns back to IDLE STATE(0000) when RELOAD is low
- all item counters are set to 10 (only 14 is visible on waveform, but hard-coded so should be no difference)
- second time RELOAD goees high, it remains in the RELOAD\_STATE for as long as RELOAD is high

 Test Case 3: IDLE\_STATE -> TRANSACT\_STATE\_1, TRANSACT\_STATE\_1 timeout




- when CARD\_IN is high, the fsm appropriately enters the TRANSACT\_STATE\_1(0011)
- the fsm stays in the TRANSACT\_STATE\_1 for 5 CLK cycles (50ns)
- since KEY\_PRESS does not go high for 50ns, there is a timeout and the fsm returns to IDLE STATE
- TRANSACT\_STATE\_1 does not alter any outputs

 Test Case 4: TRANSACT\_STATE\_1 -> TRANSACT\_STATE\_2, valid first digit entry, TRANSACT\_STATE\_2 timeout




- when CARD IN is high, the fsm appropriately enters the TRANSACT STATE 1(0011)
- the fsm receives a KEY\_PRESS signal and ITEM\_CODE of 1 before it times out
- the fsm enters TRANSACT\_STATE\_2(0100)
- the fsm stores the first digit into MSD
- TRANSACT STATE 2 does not alter any outputs
- the fsm times out after 50ns from TRANSACT\_STATE\_2 since there was no other KEY\_PRESS and ITEM\_CODE
- the fsm returns to IDLE\_STATE

 Test Case 5: TRANSACT\_STATE\_2 -> WAIT\_VALID\_SIGNAL\_STATE, valid second digit




- from TRANSACT\_STATE\_2, fsm appropriately enters the WAIT\_VALID\_SIGNAL\_STATE(0110) when KEY\_PRESS goes high and the second digit is entered
- MSD is 1 and LSD is 4, and 14 is a valid item code
- WAIT\_VALID\_SIGNAL\_STATE does not alter any outputs
- RESET and RELOAD in order to return to IDLE\_STATE for the next test case

 Test Case 6: TRANSACT\_STATE\_2 -> INVALID\_SEL\_STATE, invalid first digit entry




- from TRANSACT STATE 1, fsm receives 2 as MSD (invalid)
- from TRANSACT STATE 2, fsm receives 0 as LSD
- there is no item 20, thus the item code is invalid
- fsm does not go to WAIT\_VALID\_SIGNAL\_STATE and goes to INVALID\_SEL\_STATE(0101) instead
- INVALID SEL is set to high
- fsm immediately returns to IDLE\_STATE

 Test Case 7: TRANSACT\_STATE\_2 -> INVALID\_SEL\_STATE, invalid second digit entry




- from TRANSACT STATE 1, fsm receives 1 as MSD
- from TRANSACT STATE 2, fsm receives 10 as LSD (invalid)
- the second digit cannot be two digits long, thus the item code is invalid
- fsm does not go to WAIT\_VALID\_SIGNAL\_STATE and goes to INVALID\_SEL\_STATE(0101) instead
- INVALID SEL is set to high
- fsm immediately returns to IDLE\_STATE

 Test Case 8: WAIT\_VALID\_SIGNAL\_STATE -> INVALID\_TRAN\_STATE, WAIT\_VALID\_SIGNAL\_STATE timeout




- with an appropriate item code of 14, fsm enters the WAIT\_VALID\_SIGNAL\_STATE
- for 50ns, there is not VALID\_TRAN input, and there is a timeout
- the fsm instead enters the INVALID\_TRAN\_STATE(1000) where it sets FAILED\_TRAN to high
- the fsm immediately returns to IDLE\_STATE

 Test Case 9: first successful vending of item 14, VEND\_STATE timeout




- appropriate item code of 14 is entered
- goes from TRANSACT\_STATE\_2 to WAIT\_VALID\_SIGNAL\_STATE
- fsm recieves VALID TRAN signal, enters VEND STATE
- during VEND\_STATE, fsm decrements item 14's counter from 10 to 9, and sets VEND to high
- fsm waits 50ns in VEND\_STATE for the DOOR\_OPEN signal, but no such signal comes
- fsm times out and returns to IDLE\_STATE, but this was a successful vend

Test Case 10: 11th vending of item 14

 

- all 10 items of item 14 has been vended, and the counter is at 0
- the fsm tries to vend item 14 for the 11th time
- from TRANSACT\_STATE\_2, item code received is 14, and the fsm enters INVALID SEL STATE(0101)
- from INVALID\_SEL\_STATE, fsm returns to IDLE\_STATE

 Test Case 11: returning to RESET\_STATE\_ from a non-RELOAD\_STATE or IDLE\_STATE



 successfully enters RESET\_STATE(0001) from WAIT\_VALID\_SIGNAL\_STATE(0110)

## Conclusion

The design of vending\_machine includes no submodules, and deals with current\_state, next\_state, counter, and outputs in its own always block. The changes made to current\_state and counter are offset in time by using a posedge and a negedge. The next\_state is either a function of inputs and current state or a function of inputs, counter, and current state.

The most difficult part of this project was figuring out the timing, and how to really implement the counter in a way that the states would time out after 50ns. There were many more state transitions than project 3, but the transitions were much easier to visualize and implement compared to project 3. The given four always block setup made implementation possible.

I cannot think of a way to improve this project. The project was explained in more detail and guided compared to project 3, and was overall less stressful to implement.